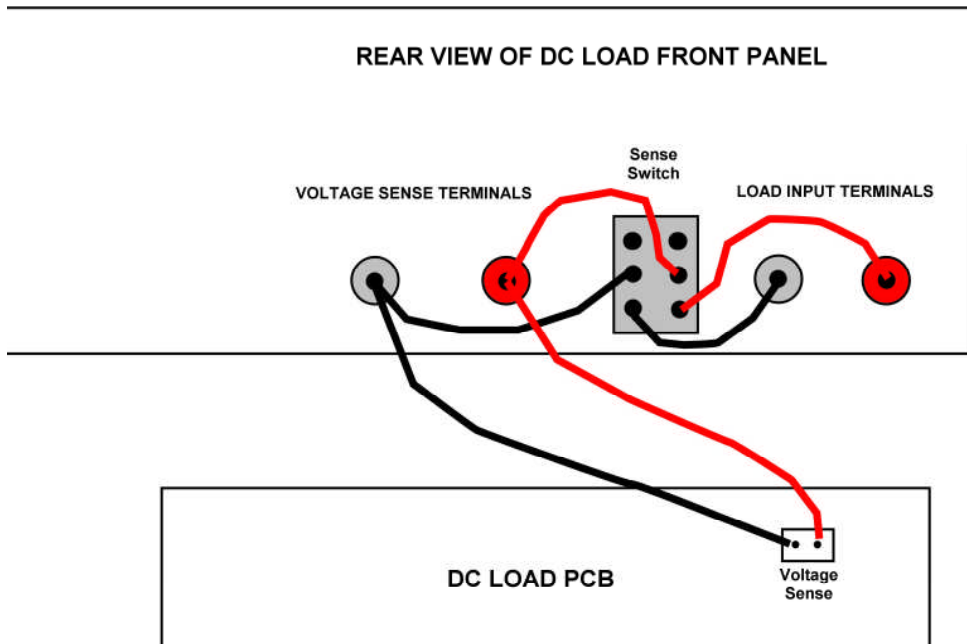


SCULLCOM HOBBY ELECTRONICS

ELECTRONIC DC LOAD Version 9.2

Wiring diagram of Voltage Sense Switch wiring



The Voltage Sense switch is used to connect the LOAD input connections directly to the VOLTAGE SENSE input on the PCB when no Voltage Sense Input Wires are used.

Normally when Voltage Sense Input is applied to the Sense terminals on the front panel the Sense Switch is OFF.